## www.hifisonix.com

## New Hifisonix Ripple Eater PSU aka 'REP'

This low-noise PSU is designed specifically for stereo class A amplifiers up to 30W RMS per channel output. It can also be used with stereo class AB amplifiers up to 100W per channel. If you adhere to the REP wiring diagram on slide 15, you can readily achieve peak hum and mains noise levels of -110 dBr on your amplifier. The power supply rectifier and series pass transistors are designed to be screwed to the amplifier baseplate metalwork, which acts as the heatsink.

Read this entire document carefully before assembling the board.

© Andrew C. Russell 2025

## **REP Specifications**

Operating voltage range +-20V to +-63V maximum (upper limit set by capacitor voltage)

Current Draw Up to 5A continuous from each rail; 20A peak; assumes adequate heatsinking

Power dissipation At full continuous load, 12 watts per series pass device + 8 watts for the rectifier, total 32 watts

Ripple Rejection 50 Hz > 40 dB (100 reduction)

100Hz >46 dB (200x reduction) 1kHz >50 dB (300x reduction)

Ripple Rejection bandwidth for >40 dB ripple rejection: 20 Hz to 300kHz

Soft-startup time ~4 seconds 0V to 90% of final output voltage on each rail; essentially load independent

Note: For operating voltages below 35V, change R10 and R11 to 3.3k

Order a PCB for the REP by clicking on this link






www.hifisonix.com

Ripple Eater PSU aka 'REP'
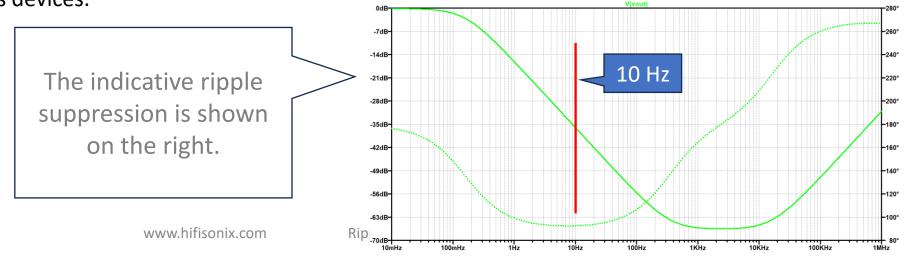
#### Hifisonix REP: General Comments

- This split voltage PSU is designed for stereo class A amplifiers up to 30W RMS output per channel and class AB amlifiers up to 100 watts per channel
- It has facilities for 4 off 35mm diameter by 10mm pin spacing capacitors, followed by a ripple eater one for each rail.
- The user can select the reservoir capacitance they want, within the constraints of the capacitor dimensions mentioned.
- The ripple eater (actually a capacitance multiplier) will drop 1.6 to 2V across each series pass element <u>at full load</u>, but effectively <u>remove all ripple components</u> (rectified AC and load induced) above ~10Hz.
- The board has been carefully laid out with a contiguous ground plan on the top copper side to ensure radiating loops and common impedance coupling are kept to an absolute minimum.
- The solder mask on the high current carrying conductors under the board is cleared, allowing builders to solder 1mm thick copper wire onto the PC traces to lower trace resistances.


This improved power supply replaces the original Hifisonix ripple eater power supply and its follow-up version that used NJW1302/1381 series pass devices.



#### **Circuit Description**

- The REP accepts either a dual or a centre tapped secondary via ACS1 through AC2E1 and uses a single bridge rectifier (D1 PB5008 45A) after which the raw DC feeds the reservoir capacitor bank comprising C2, C3, C4 and C5
- J1, located near D1, provides a convenient set of grouped connections (0V, V+ and AC Detect) to the Hifisonix Speaker Protection Board if you decide to use that. R1 is included to limit the current should the AC detect signal inadvertently be shorted to ground.
- Only the positive half of the circuit will be described here the negative half is exactly the same.
- R4 and C6 form a low pass filter (fo~.072Hz) which then feeds into the base of Q1 (TTC004B) via base stopper R6 (100 Ohm).
- The emitter of Q1 feeds into the base of Q3, a 15A bipolar transistor (NJW3281), with R8 providing the base emitter bleeder resistor.
- The ripple eater stage feeds the output connectors (J2 and J3 V+), while R10 (4.7k) and LED D4 provice power indication.
- Diode D8 clamps the V+ rail to -0.7V if the rails power up or down unevenly. Note, this diode is designed only to handle short transient spikes of a few 10s of milliseconds.
- Diode D6 ensures Q3 emitter to base voltage cannot become reverse biased this is an unlikely event, but the eventuality is catered for.
- D2 allows C6 to rapidly discharge on power down. This is important because high currents and high collector to emitter voltages on Q3 stress the device. When C6 initially charges up through R4, the output voltage comes up slowly and therefore the load current on the output.
- R2 provides a further discharge path for when the voltage across C6 is < 0.7V.

#### **REP Schematic**

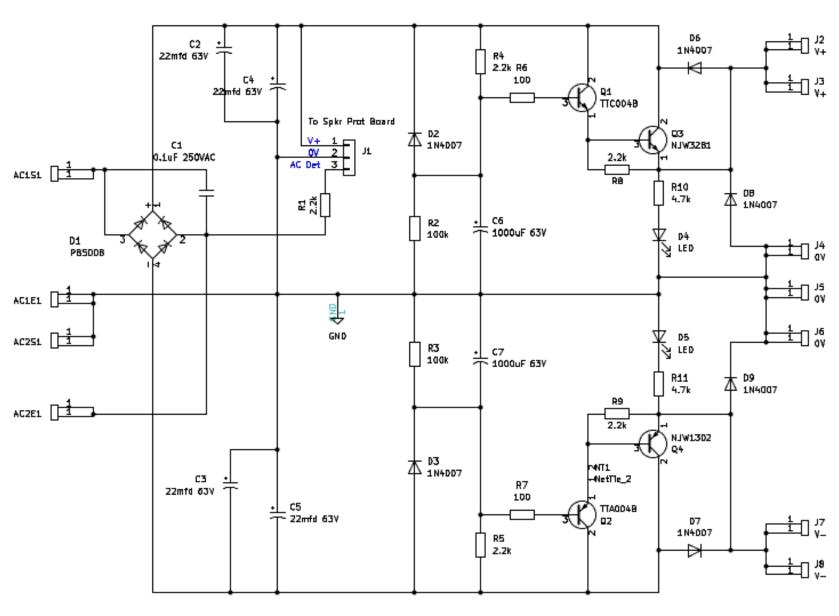

This ripple eater PSU can be used for amplifiers up to +-63VDC supply rails.

The peak current draw from this supply must not exceed 2DA.

For C2 through C5, the PCB will accept 35mm diameter capacitors with 2 plns spaced at 10mm.

For class A ampliflers, 33mfd to 47mfd is recomended.

For class AB amplifiers, 22 mfd to 33 mfd is recomended.

Do NOT exceed the maximum capacitor rated voltages!

O H1

D <sup>H2</sup>

**○** H3

O H4

#### Ripple voltage into the ripple eater – estimator. The REP output ripple will be >40 dB lower above 10Hz and 46 dB above 100Hz

DC Load current per										
rail	0.01	0.015	0.018	0.022	0.027	0.033	0.047			
0.5	0.50	0.33	0.28	0.23	0.19	0.15	0.11			
1.5	1.50	1.00	0.83	0.68	0.56	0.45	0.32			
2.5	2.50	2.50	2.50	2.50	2.50	2.50	2.50			
3.5	3.50	3.50	3.50	3.50	3.50	3.50	3.50			
4.5	4.50	3.00	2.50	2.05	1.67	1.36	0.96			
5.5	5.50	3.67	3.06	2.50	2.04	1.67	1.17			

These figures are the pk~pk ripple
voltages at the reservoir capacitor
output <i>before the ripple eater stage</i> .
The ripple eater will suppress this ripple
hy 46 dB at 100Hz and 50 dB at 1kHz


Resevoir capacitance in farads

_	
	You can estimate the pk~pk ripple voltage at the rectifier + reservoir capacitor output from

$$V_{pp} = rac{I_{load}}{2 \cdot f_{in} \cdot C}$$

	Resevoir capacitance in farads per rail 60 Hz case							
DC Load								
current per								
rail	0.01	0.015	0.018	0.022	0.027	0.033	0.047	
0.5	0.42	0.28	0.23	0.19	0.15	0.13	0.09	
1.5	1.25	0.83	0.69	0.57	0.46	0.38	0.27	
2.5	2.08	2.08	2.08	2.08	2.08	2.08	2.08	
3.5	2.92	2.92	2.92	2.92	2.92	2.92	2.92	
4.5	3.75	2.50	2.08	1.70	1.39	1.14	0.80	
5.5	4.58	3.06	2.55	2.08	1.70	1.39	0.98	
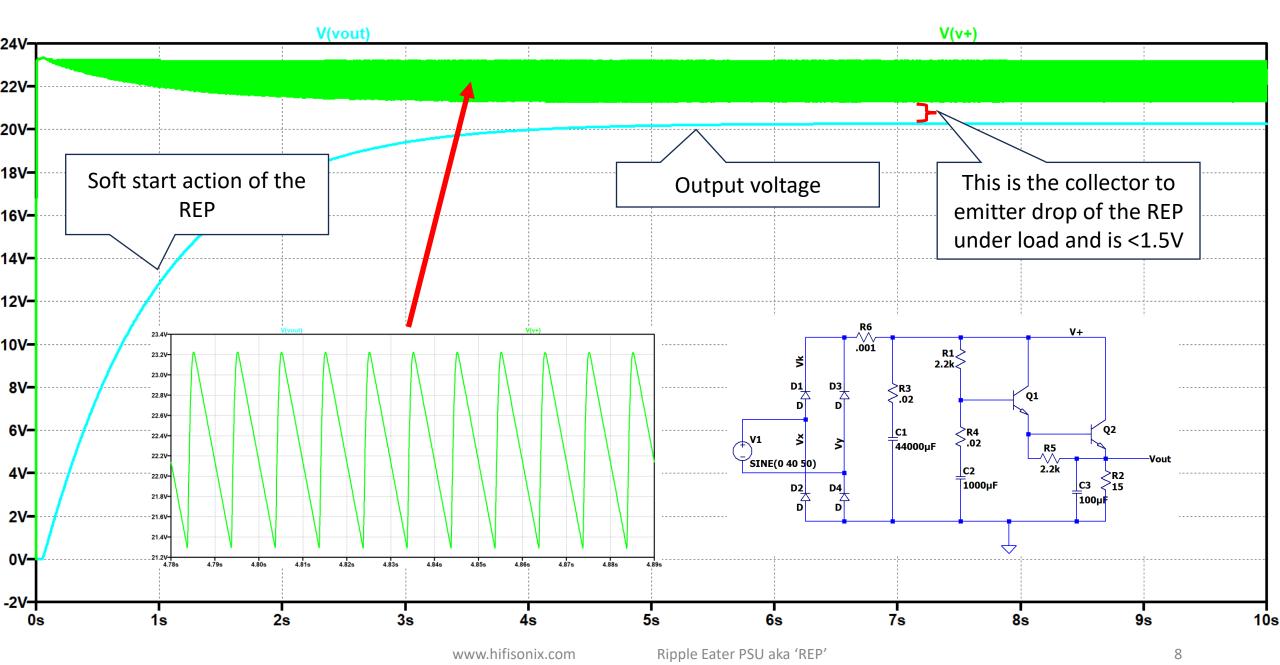
#### Sim of output ripple vs input ripple for 5A load using a 22mfd reservoir capacitor at 50 Hz



#### Assembling the PSU

- The assembly of the board is straightforward, but note the following with respect to the power supply and inrush controller PCB.
- Mount all the components except the main bridge rectifier D1, Q3 and Q4
- Tightly screw the M4 x 10mm + M4 lock washer standoffs to the PCB using 4 off M4 x 8mm machine screws. The lock washer must go to the component side of the PCB. Do not use longer or shorter screws.
- Next, bend D5 and Q3 and Q4 leads up at 90 degrees towards the front of the devices at the point on the lead frame where the leads thin.
- Feed the leads into the mounting hole from the bottom.
- Place the PCB with the loose D1, Q3 and Q4 on a FLAT surface
- Make sure the M4 standoffs are flat on the surface, and then ensure D1 is parallel to the edge of the PCB and completely flat on the resting surface before soldering it in position. Repeat the process for Q3 and Q4, making sure they line up with the mounting holes
- Finally, clip off any excess leads protruding through on the component side of the board.


#### Testing the PSU before powering up


- Firstly, double check the capacitors are inserted the correct way around. A mistake will be costly and shower your workspace with the capacitor innards. It will stink as well.
- Use you meter and check that the connections between J2 J3 and J4 to to J12 (V+), J14 (OV) and J17 (V-) are all open circuit; check that J9 (AC Detect) to J2, J3 and J4 is open circuit
- Measure from J4 to J2 it should read between 30k and 33k ohms
- Measure between J2 and J3 it must be open circuit
- Measure from J14 to J12 it should start at a low ohm value and increase as the capacitors charge – most important is to make sure it is not a short circuit
- Measure from J14 to J17 it should behave in a similar manner to the previous step make sure it is not a short circuit.
- If all of the above steps are ok, the board is ready for use.

#### How to mount the REP to the amplifier chassis Use M3 machine screw to secure Q3 and Q4 to the chassis. Use an insulating thermal washer between Q3 and Q4 and the amplifier base plate Use M3 machine screw to secure D1 to the 0 chassis. Use 0 **Use M4 lock washers** tab to chassis metalwork some thermal on the PCB side of the 0 grease between 35mm Diameter 35mm Diameter M4 mounting screws. 10mm pin spacing D1 tab and the 10mm pin spacing chassis. You do 1000uF 63V V- OK (c) Andrew C. Russell 2025 Do not forget to use not need to V1.0 - July 2025 insulating thermal 0 insuate D1 from washers under to TOthe chassis 0 0 3P Q3 and Q4 devices 35mm Dlameter 35mm Dlameter To Spkr Prot Board 10mm pin spacing 10mm pin spacing Low Noise Amplifier PSU + Ripple Eater www.hifisonix.com M4 x 10mm stand-off D1 and **PCB** 10mm mtg screw **Side view Chassis base plate M3 8mm** The screws must come screw Q3 and Q4 www.hifisonix.com Ripple Eater PSU aka 'REP' 11 from the underside

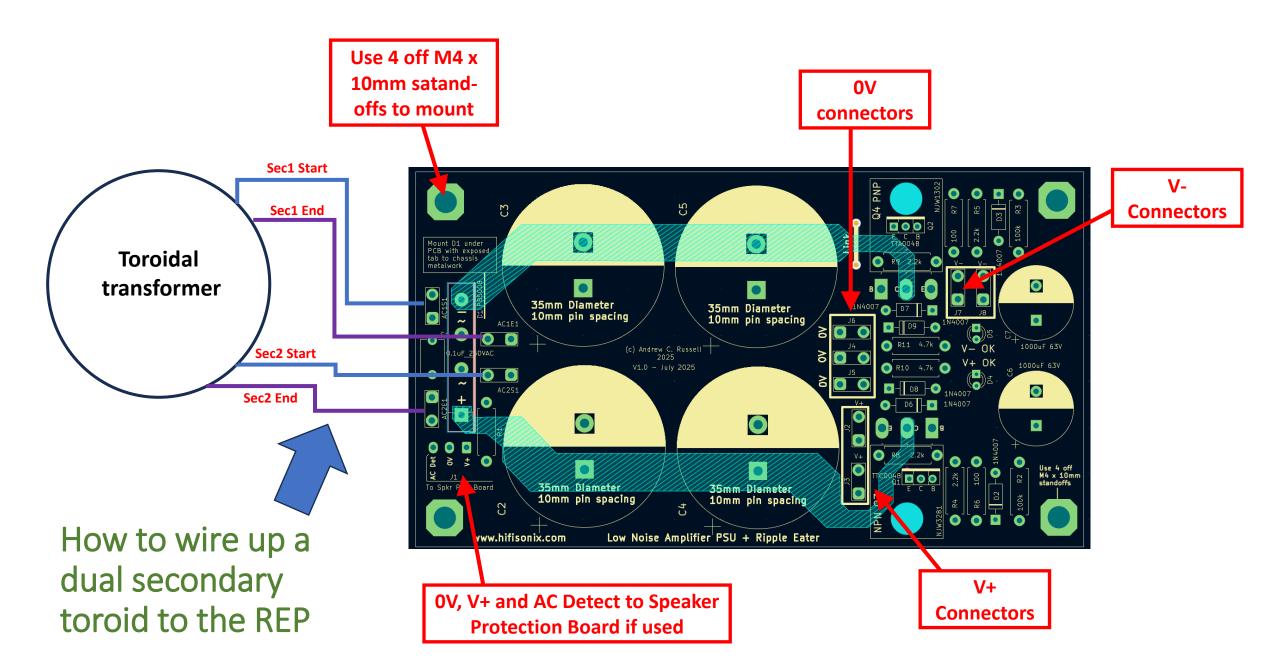
# Important

Once the REP is mounted on the chassis, check that the connection between the collectors of Q3 and Q4 to the chassis is OPEN CIRCUIT



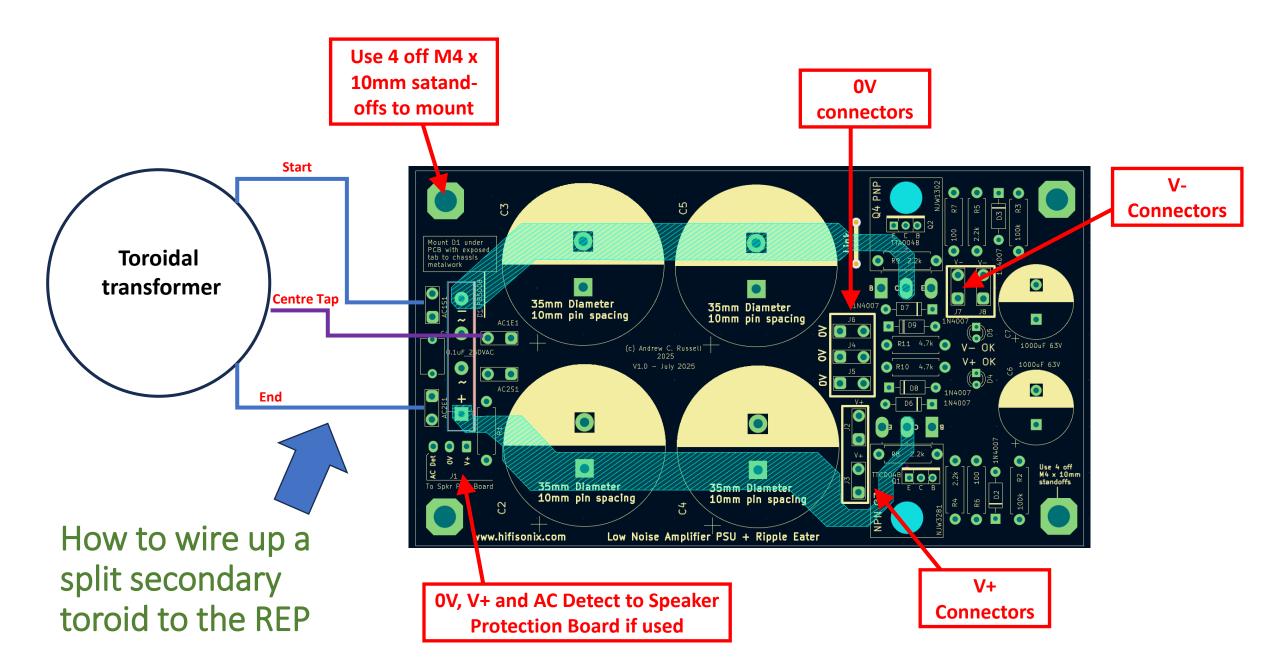

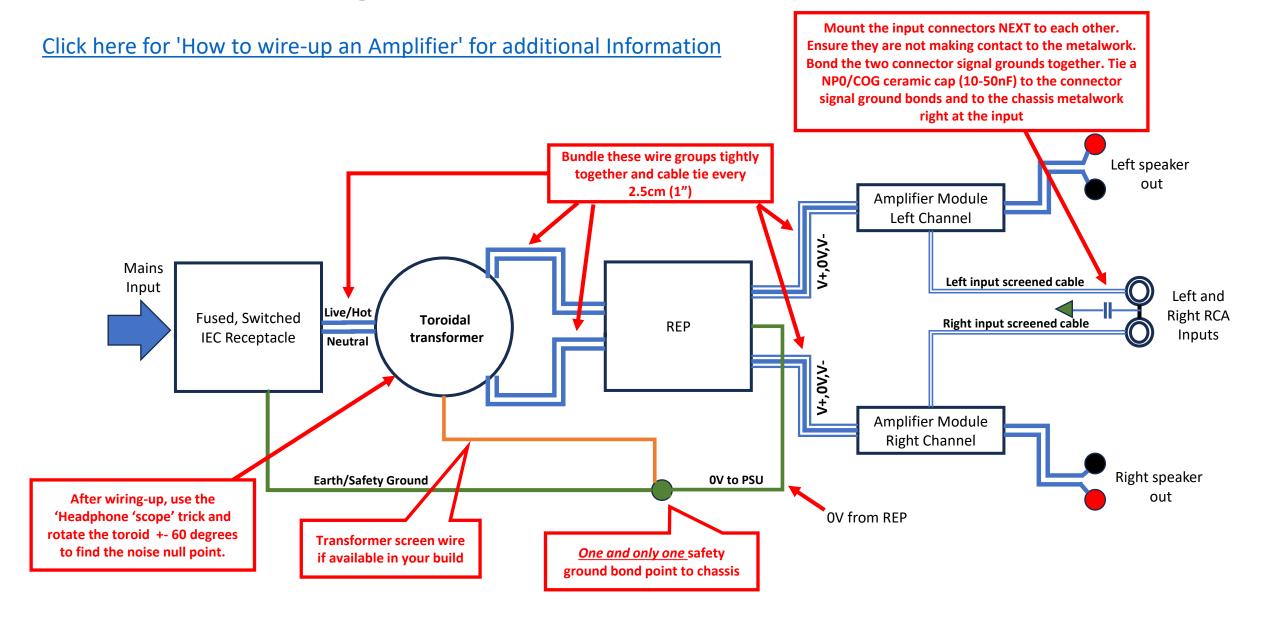
### How to use the REP to get -110 dBr noise floor





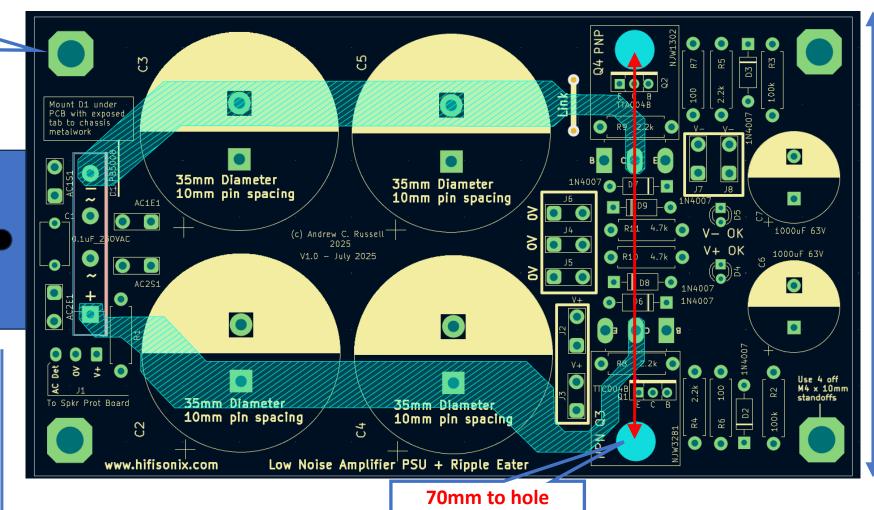D1 protrudes 15mm beyond the edge of the PCB




150mm

centres


### Examples of consumables from Amazon required for wiring up the REP.

Invest in a 6.3mm crimping tool!


HIGHLY RATED Sponsored | Based on star rating and number of customer ratings

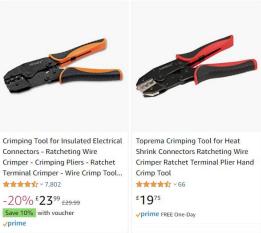

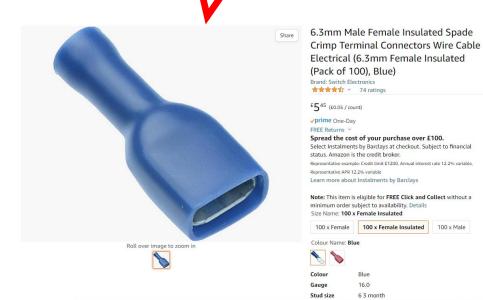Attention: only use fully insulated 6.3mm spade connectors!





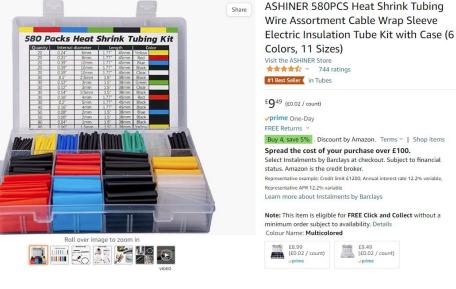



100 x Female Insulated

16.0

6 3 month

100 x Male